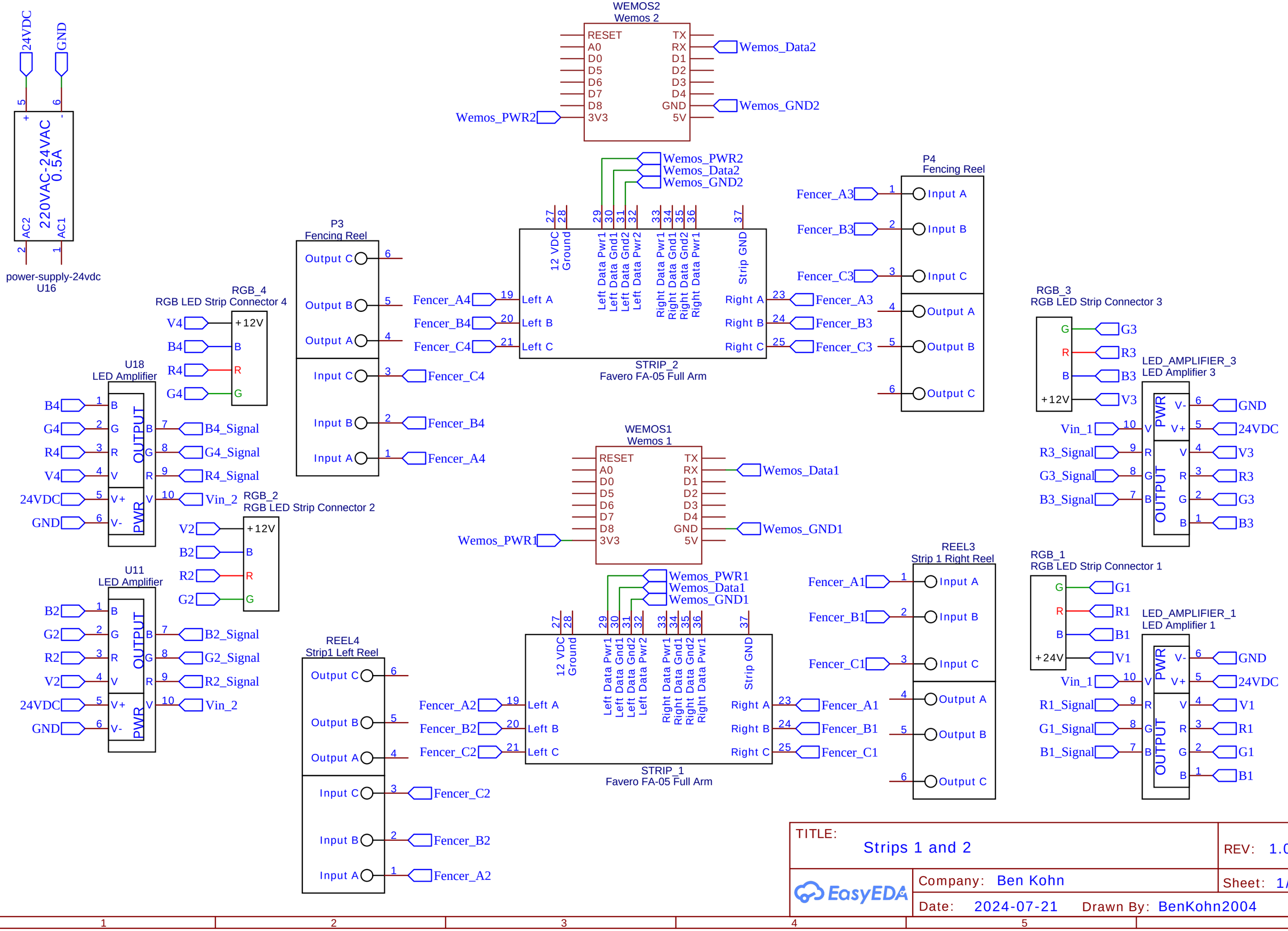


TITLE: Strips 1 and 2		REV: 1.0
EasyEDA	Company: Ben Kohn	Sheet: 1/3
	Date: 2024-07-21 Drawn By: BenKohn2004	

Note 1: Power supply from previous sheet. Not an additional power supply

24VDC
GND
5
6
+
-
220VAC-24VAC 0.5A
AC2
AC1
2
1
power-supply-24vdc
U3

WEMOS4
Wemos 4
RESET
A0
D0
D5
D6
D7
D8
3V3
TX
RX
D1
D2
D3
D4
GND
5V
Wemos_Data4
Wemos_GND4
Wemos_PWR4

P1
Fencing Reel
Input A
Input B
Input C
Output A
Output B
Output C
Fencer_A7
Fencer_B7
Fencer_C7

REEL_8
Fencing Reel 8
Output C
Output B
Output A
Input C
Input B
Input A
Fencer_C8
Fencer_B8
Fencer_A8

RGB_8
RGB LED Strip Connector 8
V8
B8
R8
G8
+12V
B
R
G

LED_AMPLIFIER_8
LED Amplifier 8
B8_Signal
G8_Signal
R8_Signal
Vin_4
24VDC
GND

RGB_6
RGB LED Strip Connector 6
V6
B6
R6
G6
+12V

LED_AMPLIFIER_6
LED Amplifier 6
B6_Signal
G6_Signal
R6_Signal
Vin_4

STRIP_4
Favero FA-05 Full Arm
12 VDC
Ground
Left Data Pwr1
Left Data Gnd1
Left Data Gnd2
Left Data Pwr2
Right Data Pwr1
Right Data Gnd1
Right Data Gnd2
Right Data Pwr1
Strip GND
Left A
Left B
Left C
Right A
Right B
Right C
Fencer_A8
Fencer_B8
Fencer_C8
Fencer_A7
Fencer_B7
Fencer_C7

RGB_7
RGB LED Strip Connector 7
G7
R7
B7
+12V
V7

LED_AMPLIFIER_7
LED Amplifier 7
Vin_3
R7_Signal
G7_Signal
B7_Signal
GND
24VDC
V7

WEMOS3
Wemos 3
RESET
A0
D0
D5
D6
D7
D8
3V3
TX
RX
D1
D2
D3
D4
GND
5V
Wemos_Data3
Wemos_GND3
Wemos_PWR3

REEL5
Strip 3 Right Reel
Input A
Input B
Input C
Output A
Output B
Output C
Fencer_A5
Fencer_B5
Fencer_C5

REEL6
Strip3 Left Reel
Output C
Output B
Output A
Input C
Input B
Input A
Fencer_C6
Fencer_B6
Fencer_A4

STRIP_3
Favero FA-05 Full Arm
12 VDC
Ground
Left Data Pwr1
Left Data Gnd1
Left Data Gnd2
Left Data Pwr2
Right Data Pwr1
Right Data Gnd1
Right Data Gnd2
Right Data Pwr1
Strip GND
Left A
Left B
Left C
Right A
Right B
Right C
Fencer_A6
Fencer_B6
Fencer_C6
Fencer_A5
Fencer_B5
Fencer_C5


RGB_5
RGB LED Strip Connector 5
G5
R5
B5
+24V
V5

LED_AMPLIFIER_5
LED Amplifier 5
Vin_3
R5_Signal
G5_Signal
B5_Signal
GND
24VDC
V5


TITLE: Strips 3 and 4	REV: 1.0
Company: Ben Kohn	Sheet: 2/3
Date: 2024-07-23 Drawn By: BenKohn2004	

South


Variables
Strip 3
Strip 4
D4
D2

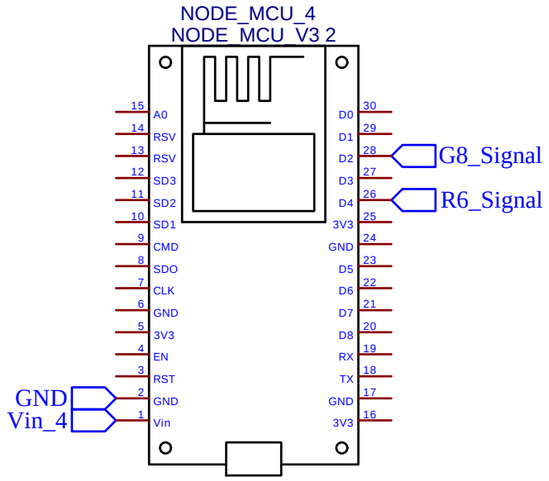

East

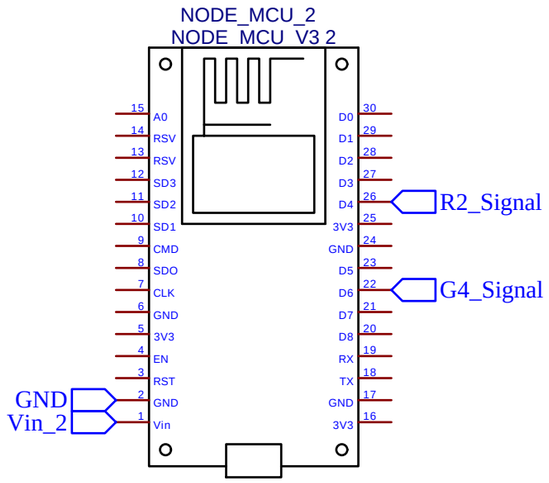


Variables
Strip 1
Strip 2
D4
D6

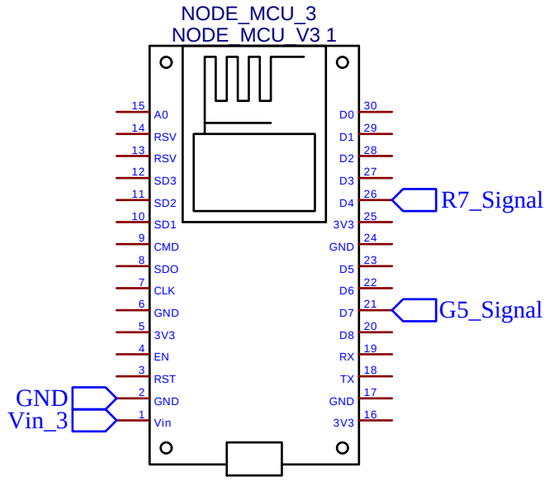

Variables
Strip 4
Strip 3
D4
D7

West

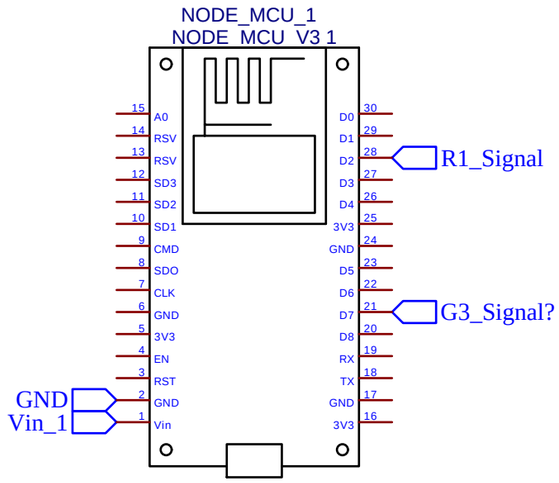

Variables
Strip 2
Strip 1
D7
?

North

TITLE: Node MCU 1,2,3,4		REV: 1.0
EasyEDA	Company: Ben Kohn	Sheet: 3/3
	Date: 2024-07-23 Drawn By: BenKohn2004	